

# Inverters in Microgrids

Giri Venkataramanan  
Department of Electrical and Computer Engineering  
University of Wisconsin-Madison

13 January 2004


[Giri@engr.wisc.edu](mailto:Giri@engr.wisc.edu)

# Outline

- Electric grid operations
- Frequency and voltage control
- Inverter based generation
- Inverter dynamic modeling
- Summary

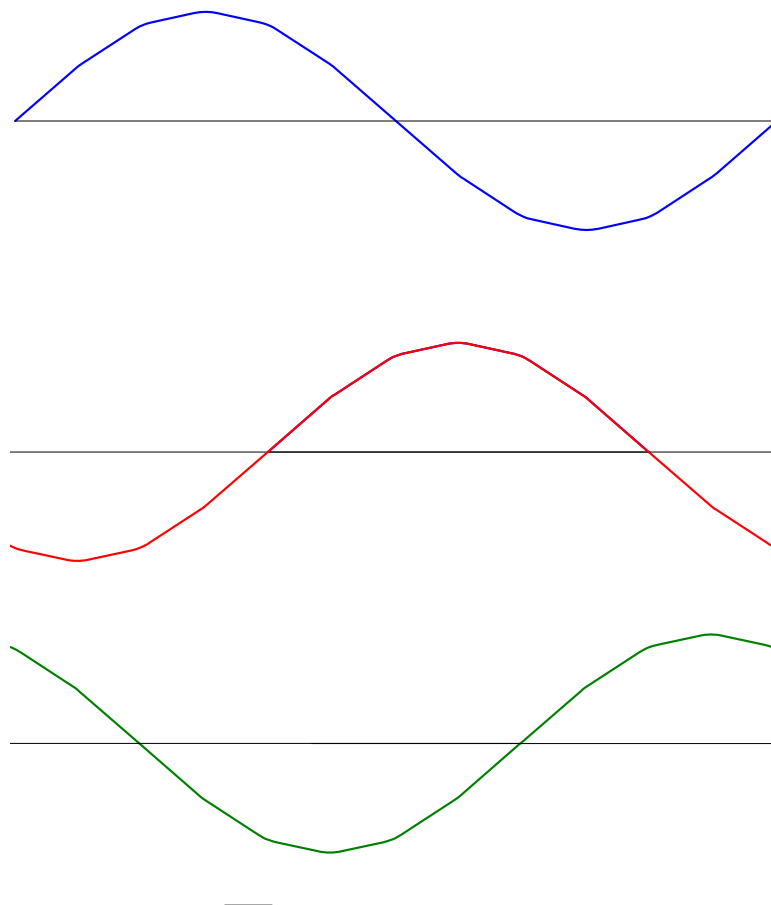
# Electrical generation

- Rotating machines
- Primarily synchronous machines
- Three phase ac output


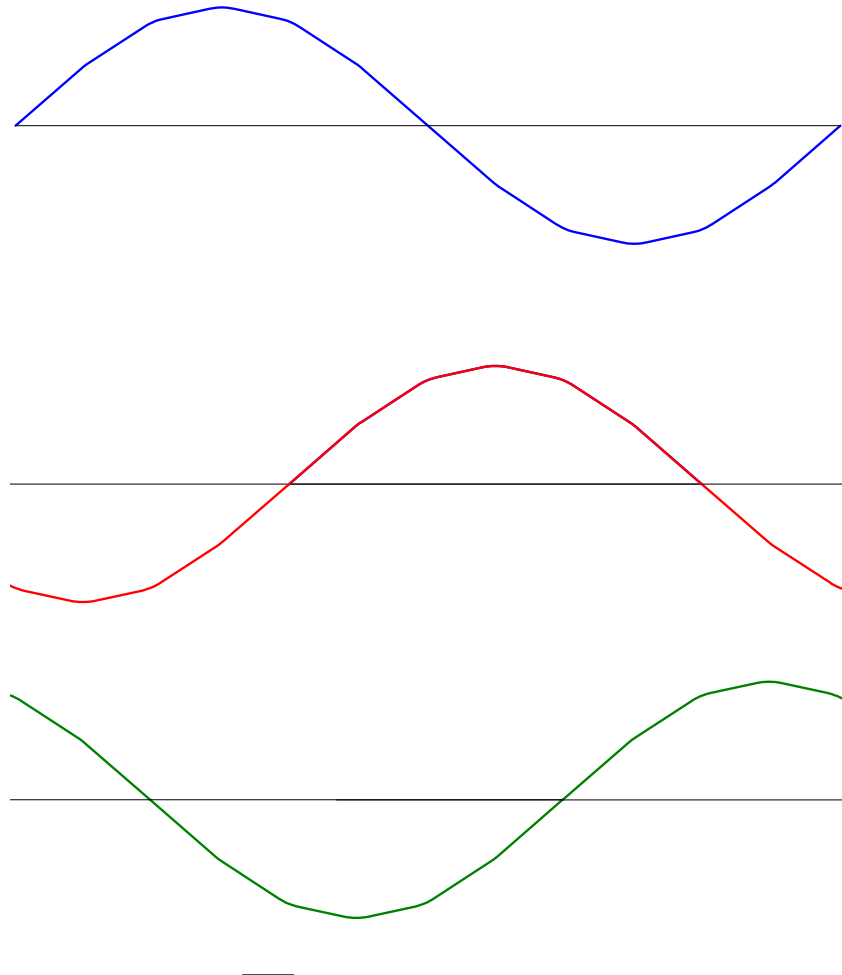
# Alternators

- Frequency  
Tied to the speed of the shaft
- Voltage  
Tied to the field excitation



# Frequency Regulation (lone machine)

- Shaft speed
  - mechanical shaft power equal to electrical load power + losses
- Speed governors
  - Measure shaft speed
  - Adjust energy (fuel) input to increase or decrease speed

# Frequency Regulation (Grid)

- Cannot have several machines trying to control speed set point locally with zero error – lead to chaos
- Allow all but one machine to have set-point errors
- All machines work on a dispatched power set point, speed follows the master
- Master machine follows the load power demand and regulates the frequency

# Voltage Regulation (lone machine)

- Field regulator

  - Measure terminal voltage

  - Adjust field excitation input to increase or decrease voltage

- Field excitation

  - Reactive power output equal to reactive power demand of load

## Voltage Regulation (Grid)


- Need appropriate voltage set points
- Improper set-points will lead to circulating currents between machines
- Typically local reactive power control loops




# Distributed Generation

- Conventional reciprocating engines
  - Wind generators
  - Photovoltaics
  - Microturbines
  - Fuel cells
  - Wave energy
- 
- Significant fraction of generation in the future


# Distributed Generation

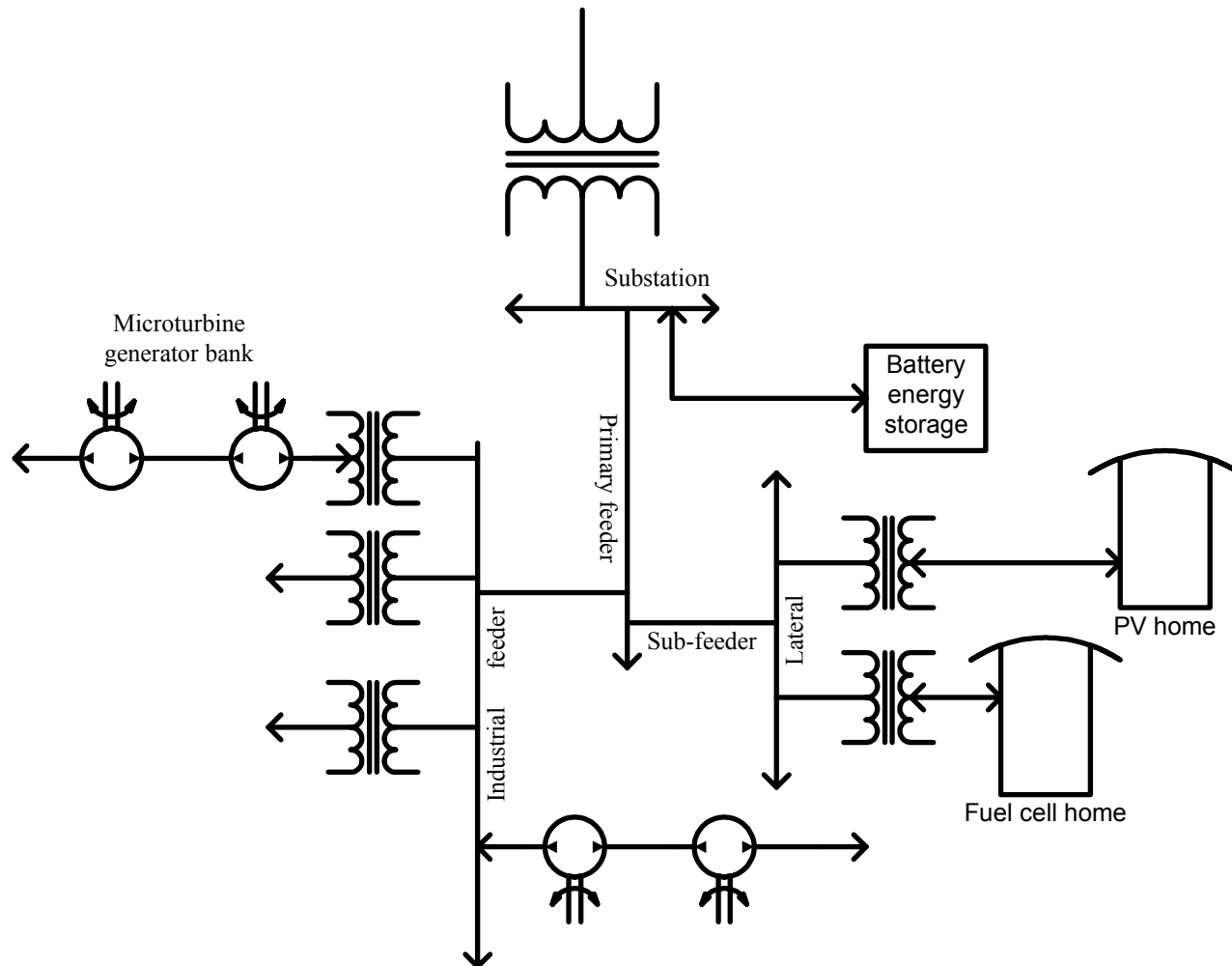



# Inverter embedded generation

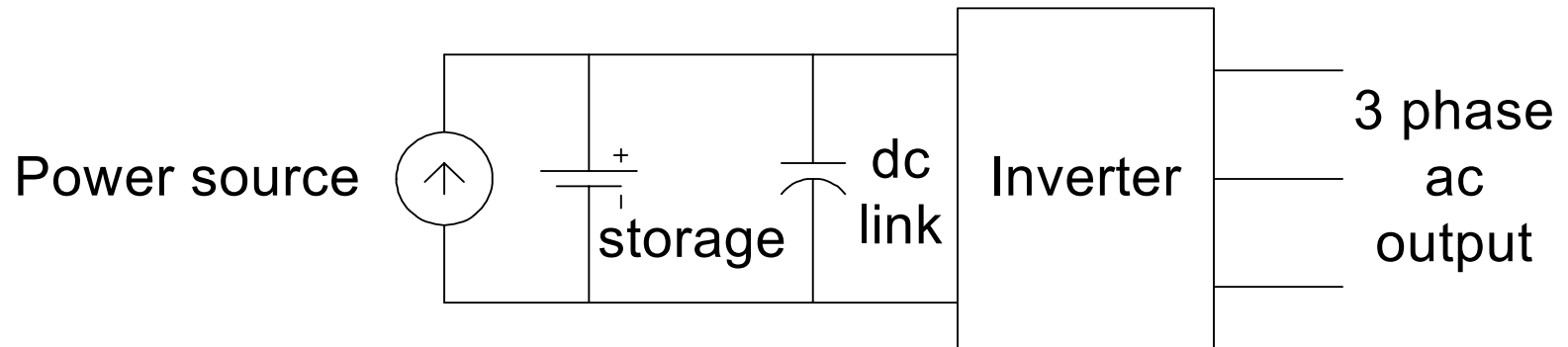



# Inverter details

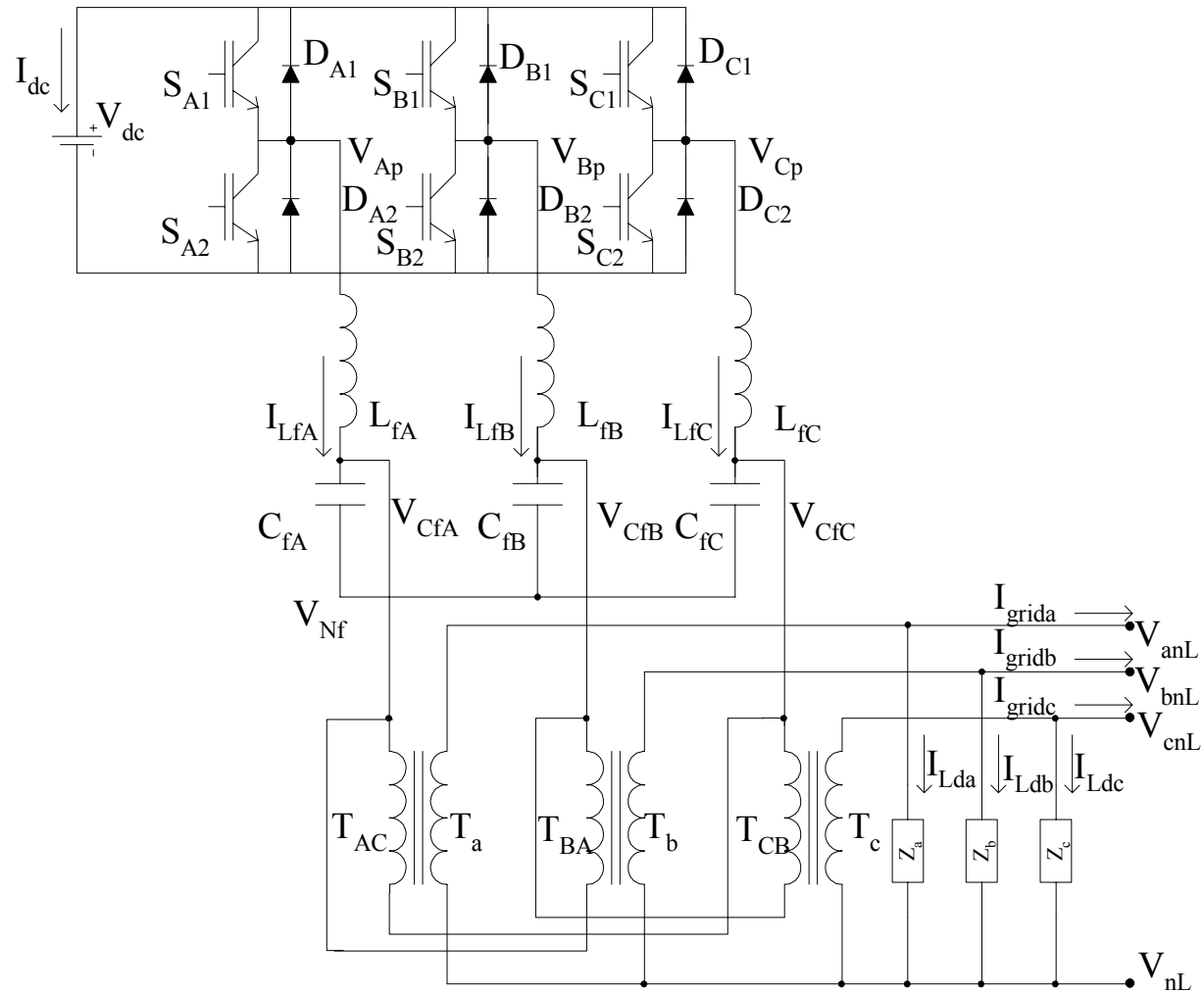

# PWM Synthesis – A, B & C phases

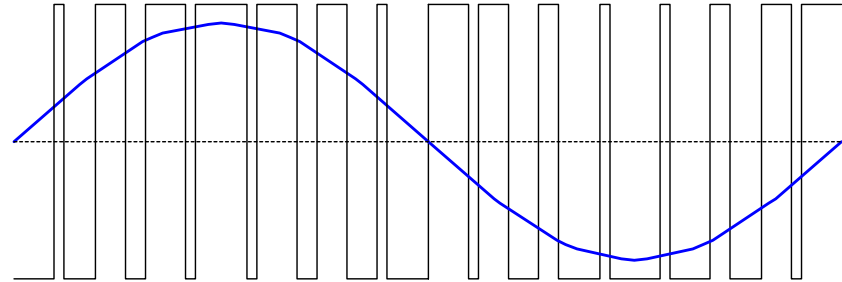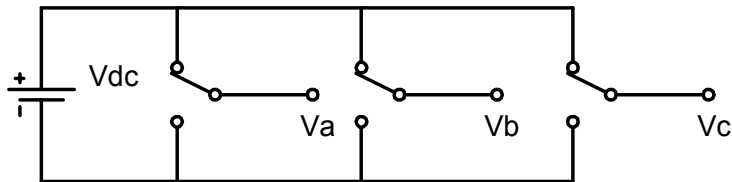

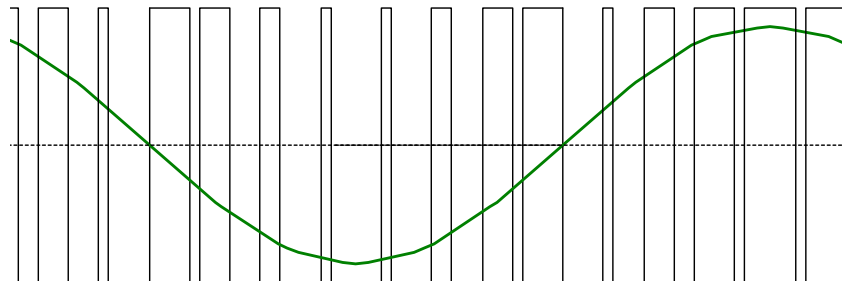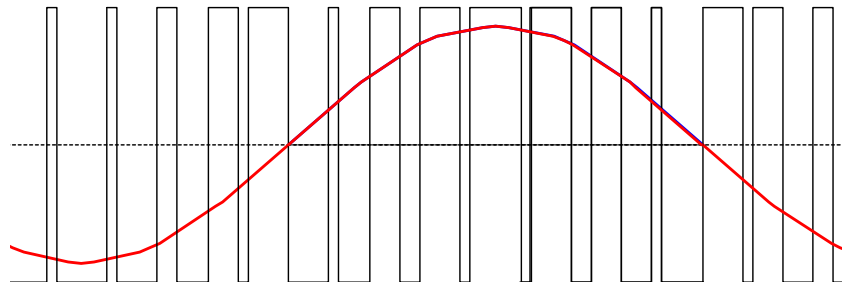- Phase shift between waveforms may be varied
- Amplitude of waveforms may be dissimilar
- All the three phase voltages could have an average  $V_{dc}/2$  common mode voltage
- Causes a neutral shift
- Will cancel out in the line-line voltages




# Microgrid Energy and Power Quality Management Functions

- Load profile control
  - Source utilization
  - Peak-shaving
  - Reactive power injection
- 
- POL voltage control
  - Voltage imbalance correction

# Key Control Issues

- Power flow control
  - Frequency control
  - Local voltage control
  - Reactive power control
- 
- Power sharing
  - Frequency matching
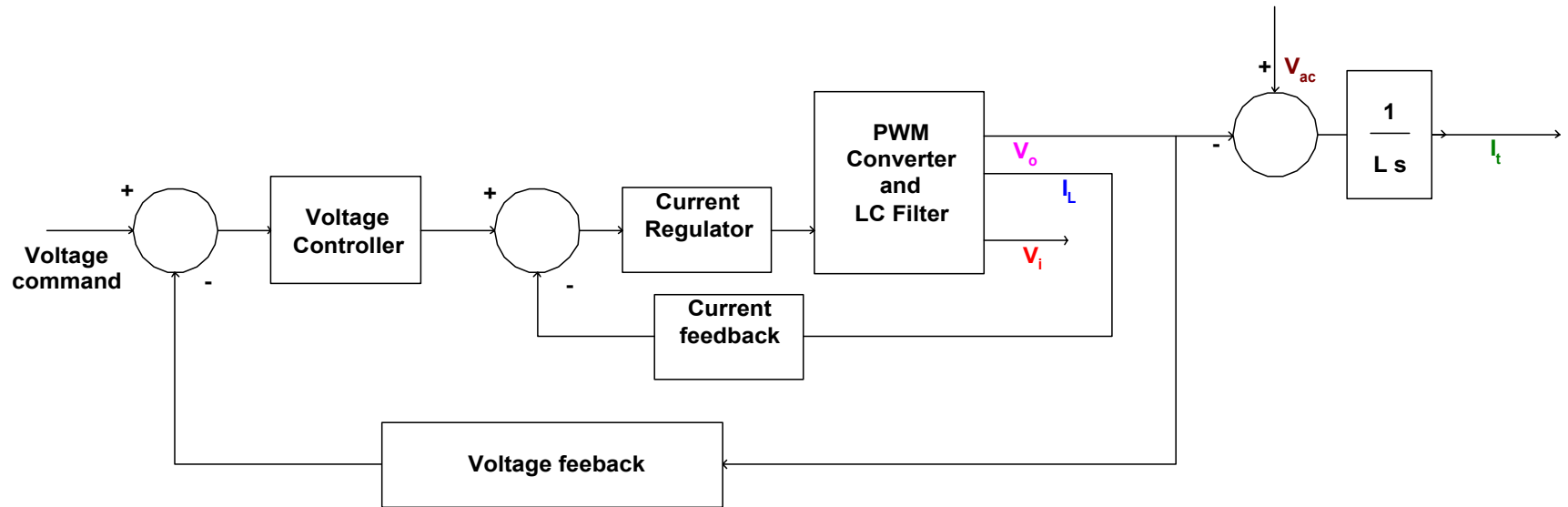
# Typical controller structure (classical)







# Typical Control Trend Today

- Operate as a balanced current source under utility connected operation
- Operate as a balanced voltage source under stand-alone operation
- Interchange from one mode to another requires anywhere between 10 seconds and 30 minutes
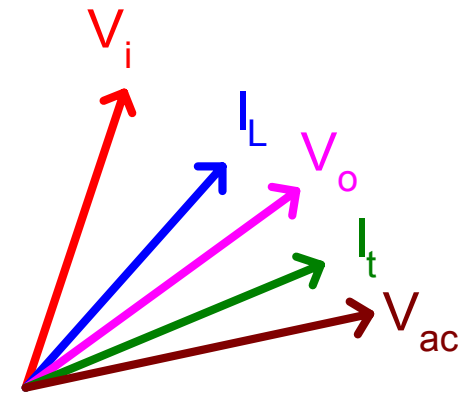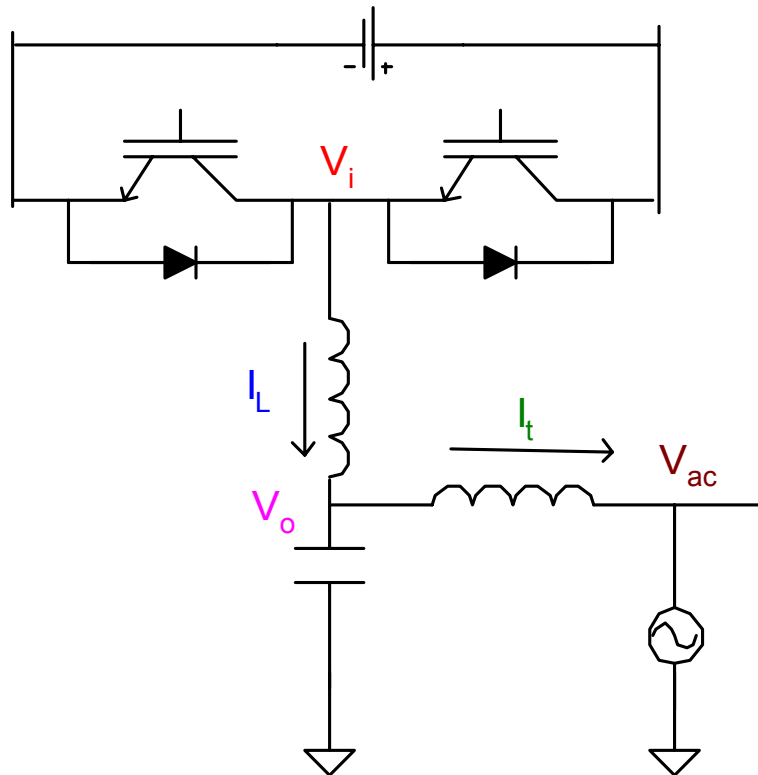
# Single line equivalent circuit and phasor diagram



- $V_{ac}$  – PCC voltage
- $V_o$  – Point of Connection (POC) Voltage


# Power throughput of inverter

$$P = \frac{V_{ac} V_o}{X_t} \sin \delta$$


$$Q = \frac{V_o^2}{X_t} - \frac{V_{ac} V_o}{X_t} \cos \delta$$


- Angle between  $V_{ac}$  and  $V_o$  determines power flow
- Magnitude of  $V_o$  determines reactive power flow

# Inverter controls

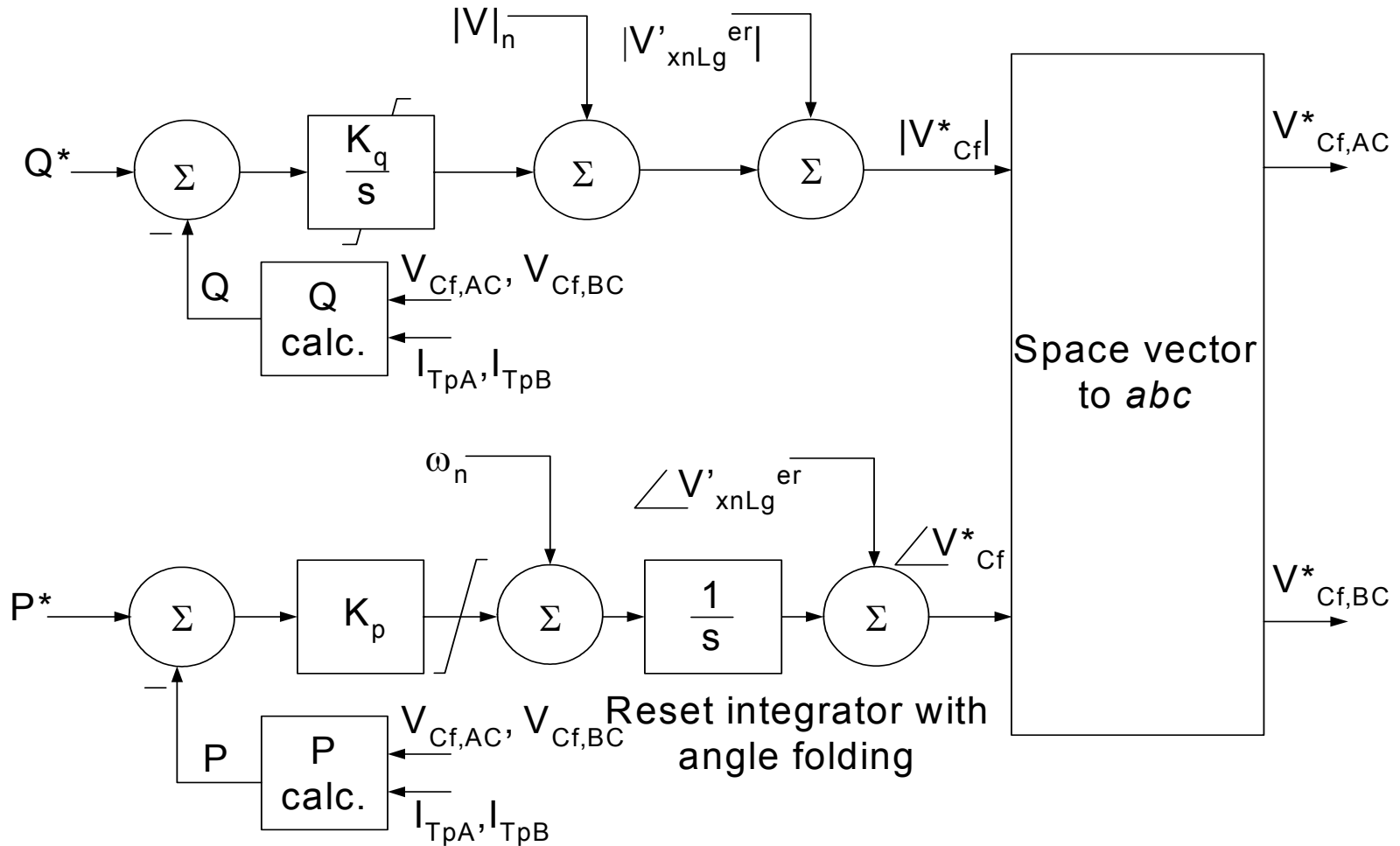


# Laboratory scale microgrid

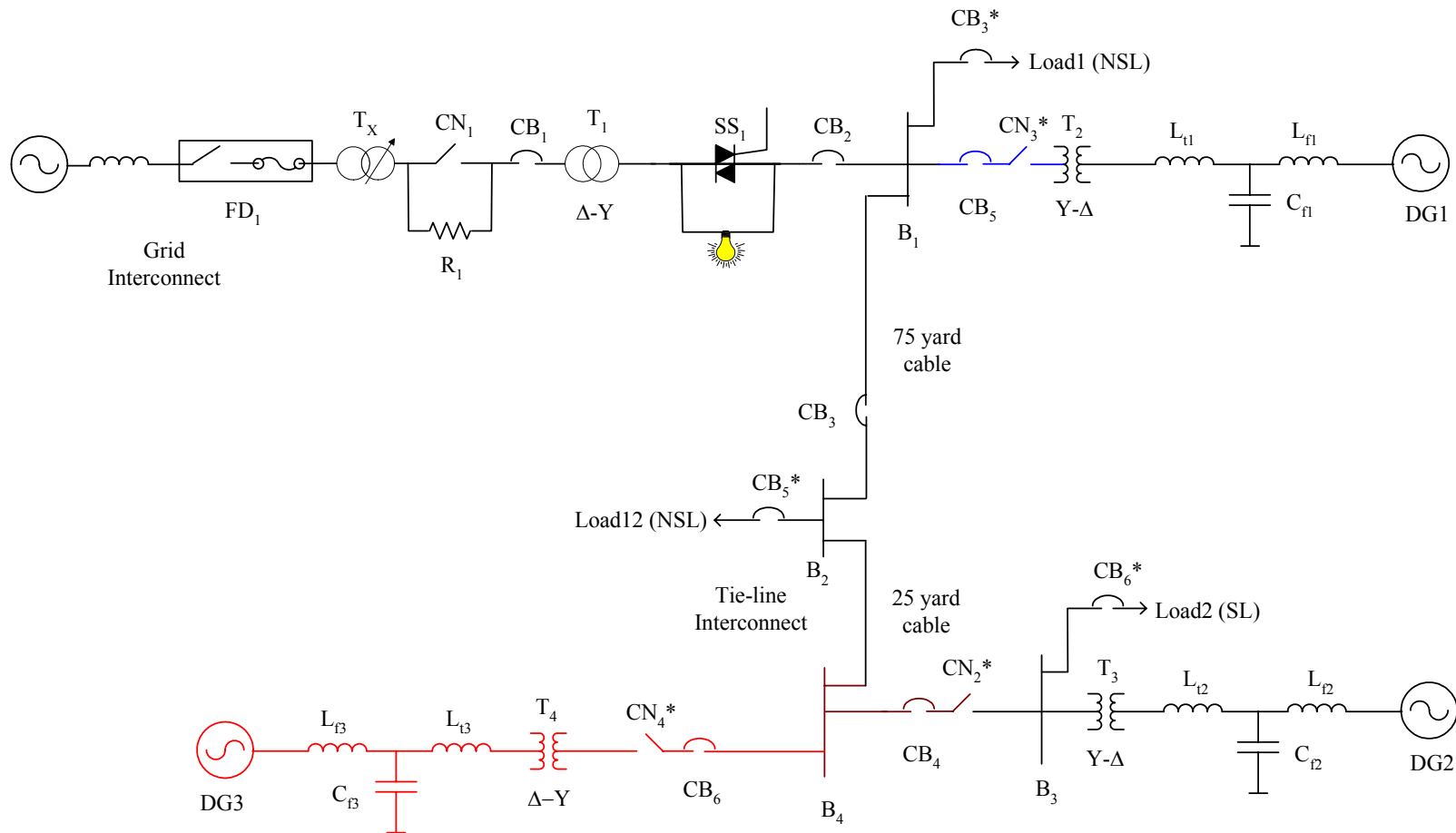

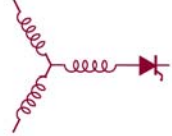
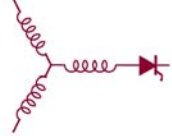
# Laboratory scale microgrid hardware details






# Laboratory scale microgrid hardware details



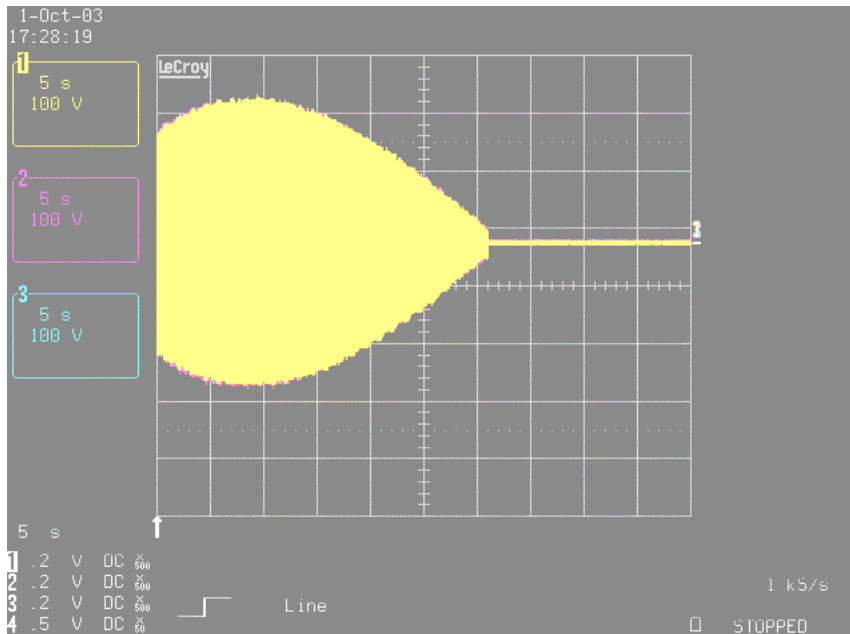
# Laboratory scale microgrid hardware results




Synchronization to grid  
'beat voltage'

P and Q transients

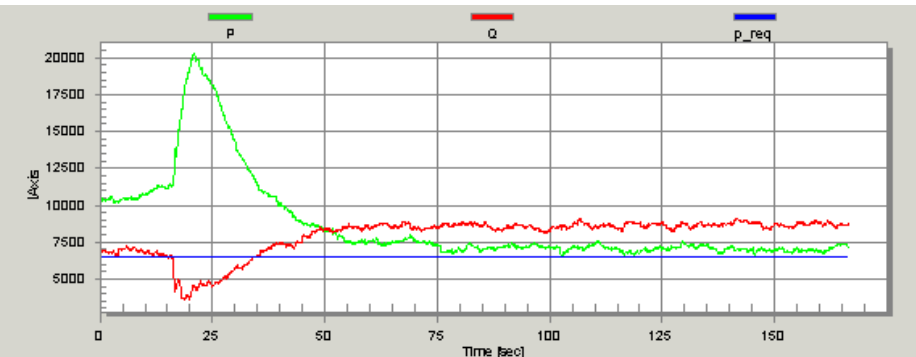



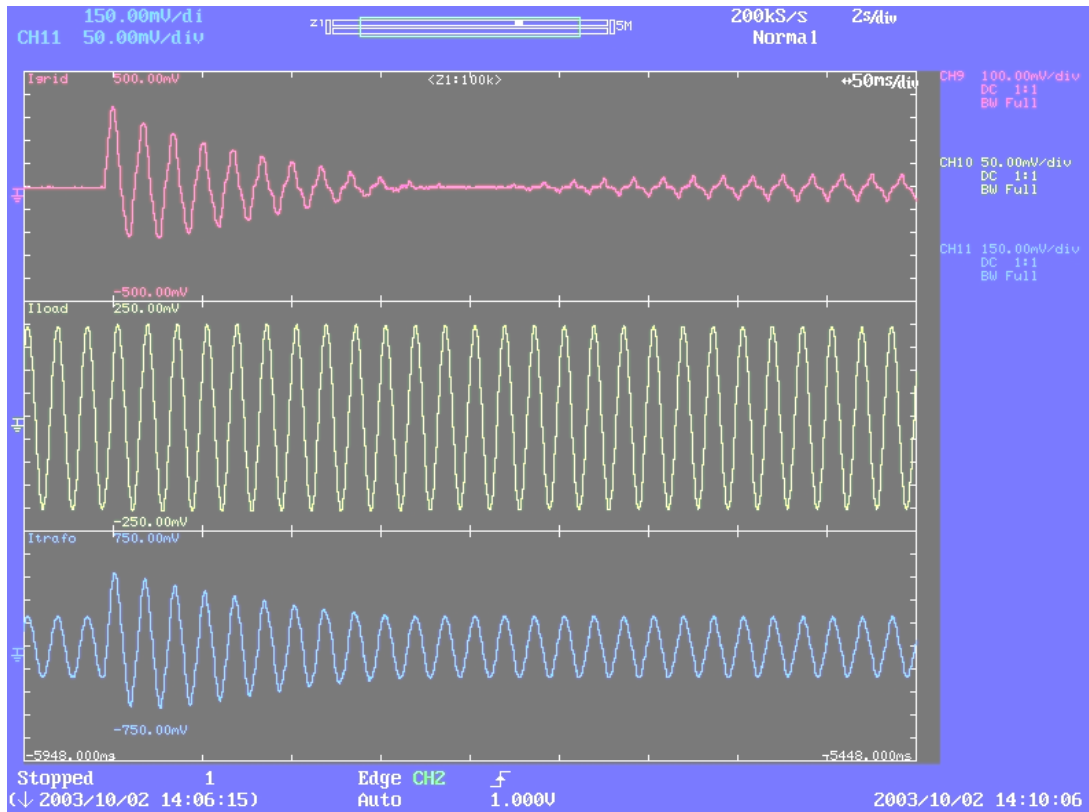
# Laboratory scale microgrid hardware results



Synchronization to grid

Voltage and current waveforms

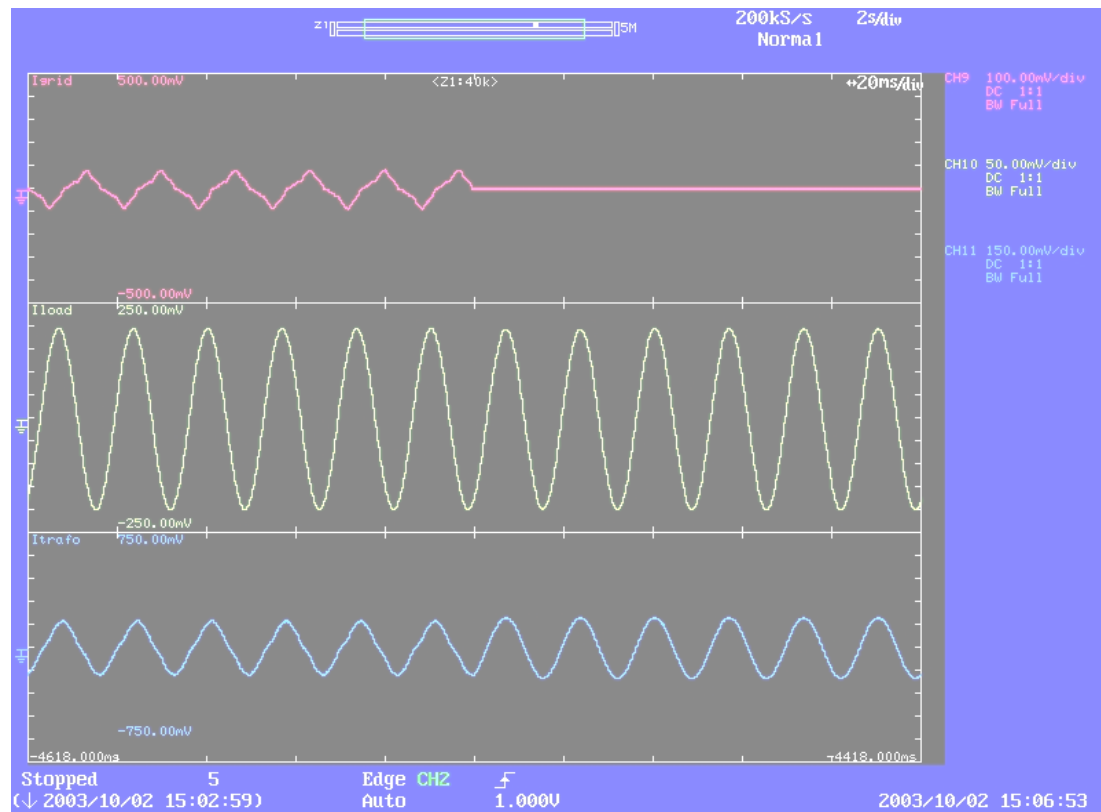
# Laboratory scale microgrid hardware results



Disconnection from grid


Voltage and current waveforms
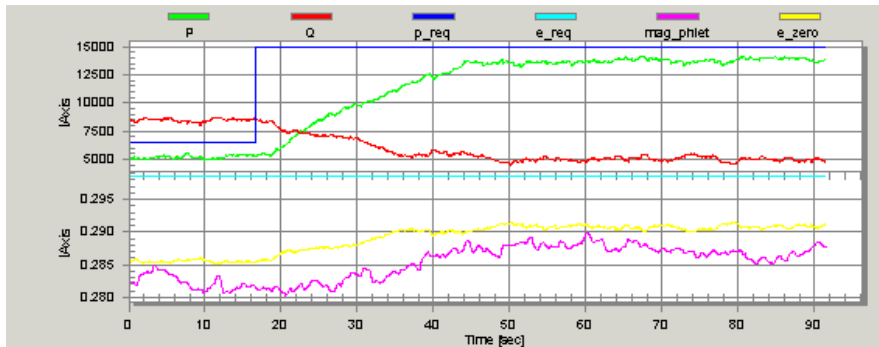
# Laboratory scale microgrid hardware results




Step response of power


Voltage and current waveforms

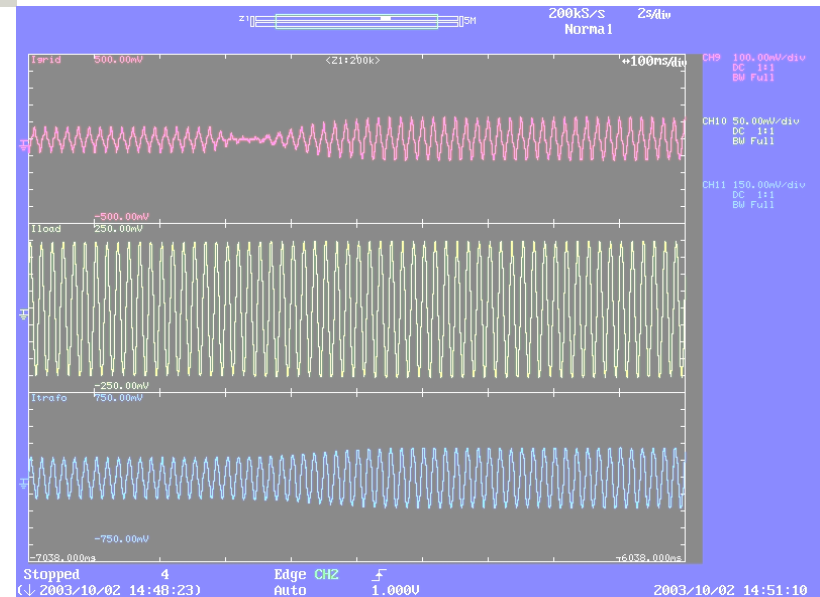

# Computer simulations

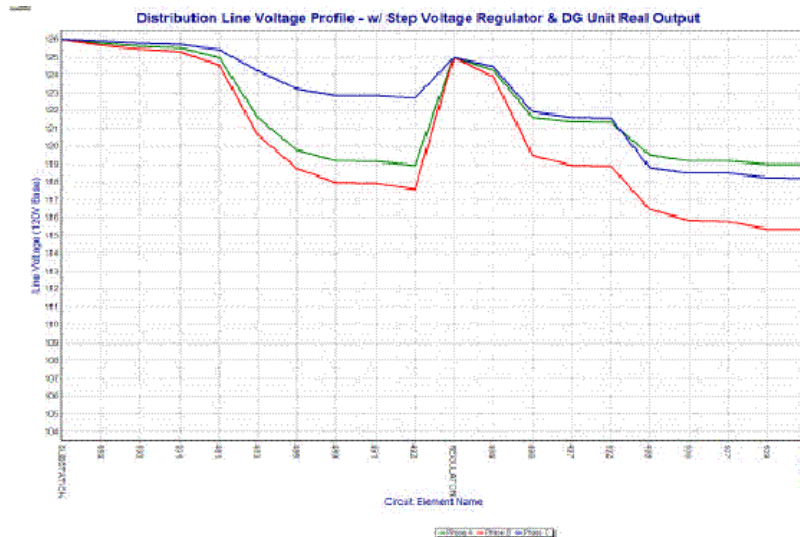

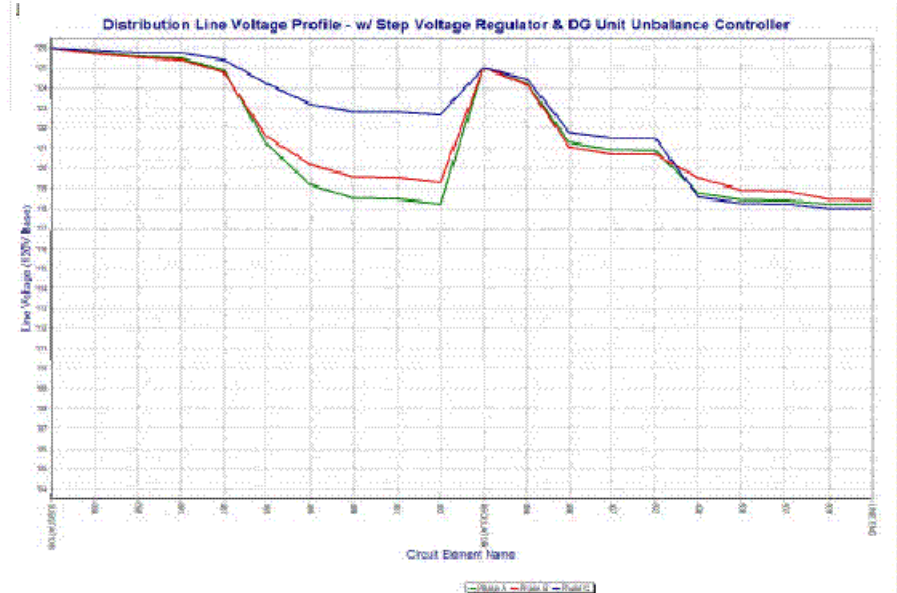Voltage profile along an unbalanced distribution feeder with conventional dg control



Voltage profile along an unbalanced distribution feeder with unbalanced dg control

## Modeling objectives

- Need to model dynamic properties
- Control input and real power flow or power angle
- Control input and reactive power flow or voltage magnitude

## Key control variables

$$m(t) = |m(t)|e^{j\angle m(t)}$$

$$v_i(t) = |v_i(t)|e^{j\angle v_i(t)}$$

$$i_L(t) = |i_L(t)|e^{j\angle i_L(t)}$$

$$v_o(t) = |v_o(t)|e^{j\angle v_o(t)}$$

Instantaneous phase quantities are projections of the rotating vectors on appropriate axes

# Dynamic Equations

$$L \frac{d}{dt} i_L = v_{dc} |m| \cos(\angle m - \angle i_L) - |v_o| \cos(\angle v_o - \angle i_L)$$

$$L |i_L| \frac{d}{dt} \angle i_L = v_{dc} |m| \sin(\angle m - \angle i_L) - |v_o| \sin(\angle v_o - \angle i_L)$$

$$C \frac{d}{dt} |v_o| = |i_L| \cos(\angle i_L - \angle v_o) - \frac{|v_o|}{R}$$

$$C |v_o| \frac{d}{dt} \angle v_o = |i_L| \sin(\angle i_L - \angle v_o) - \frac{|v_o|}{R}$$

## Steady state operating condition

$$0 = V_{dc} |M| \cos(\angle M - \angle I_L) - |V_o| \cos(\angle V_o - \angle I_o)$$

$$L |I_L| \omega = V_{dc} |M| \sin(\angle M - \angle I_L) - |V_o| \sin(\angle V_o - \angle I_L)$$

$$0 = |I_L| \cos(\angle I_L - \angle V_o) - \frac{|V_o|}{R}$$

$$C |V_o| \omega = |I_L| \sin(\angle I_L - \angle V_o) - \frac{|V_o|}{R}$$



# Steady state operating condition

$$0 = V_{dc} |M| \cos(\phi_{mi_L}) - |V_o| \cos \phi_{v_o i_L}$$

$$L |I_L| \omega = V_{dc} |M| \sin \phi_{mi_L} - |V_o| \sin \phi_{v_o i_L}$$

$$0 = |I_L| \cos \phi_{i_L v_o} - \frac{|V_o|}{R}$$

$$C |V_o| \omega = |I_L| \sin \phi_{i_L v_o} - \frac{|V_o|}{R}$$

Classical phasor solution

# Small signal model at operating point

$$\dot{x} = Ax + Bu$$

$$y = Ex + Fu$$

$$u = |\tilde{m}|$$



$$x = \begin{bmatrix} |\tilde{i}_L| \\ \angle \tilde{i}_L \\ |\tilde{v}_o| \\ \angle \tilde{v}_o \end{bmatrix}$$

$$A = \begin{bmatrix} 0 & \omega I_L & \frac{-|V_o|}{LR|I_L|} & \frac{-\omega C|V_o|^2}{|I_L|^2 L} \\ \frac{-\omega}{|I_L|} & 0 & \frac{-\omega C|V_o|}{|I_L|^2 L} & \frac{-|V_o|^2}{LR|I_L|^2} \\ \frac{|V_o|}{RC|I_L|} & -\omega|V_o| & \frac{-1}{RC} & \omega|V_o| \\ \frac{\omega}{|I_L|} & \frac{1}{RC} & \frac{-\omega}{|V_o|} & \frac{-1}{RC} \end{bmatrix}$$

$$B = \begin{bmatrix} \frac{V_{dc} \cos \phi_{mi_L}}{L} \\ \frac{V_{dc} \sin \phi_{mi_L}}{L|I_L|} \\ 0 \\ 0 \end{bmatrix}$$
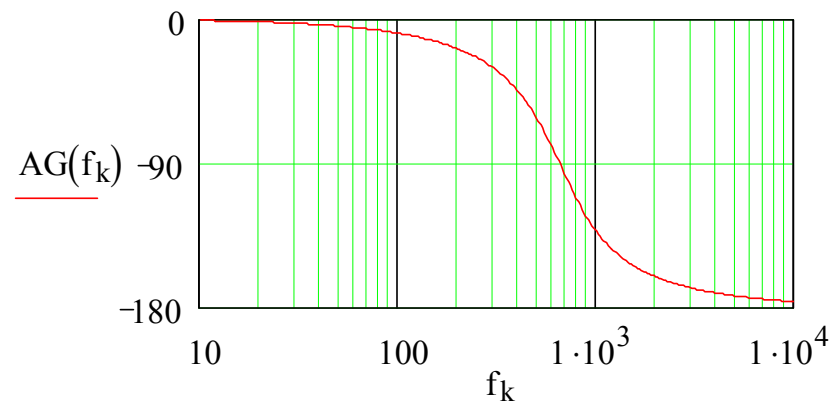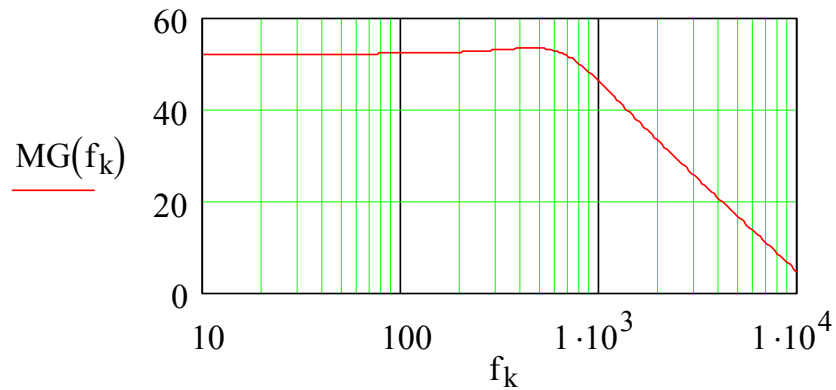
# Transfer function

- Magnitude of modulation to output voltage



# Dynamic interaction issues

- Angle input to output transfer functions
- Cross coupling transfer functions
- Selection of controllers and tuning
- Outer loop effects (Real and reactive power, droop, etc.)
- Frequency synchronization
- Interactions between multiple parallel units
- Measurement delays, uncertainties, imbalances, etc.